
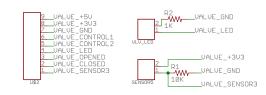
### Valve Board


Controls 1 motorized valve with sensor wires that read GND when that state (open/closed) is active. Optional status LED and sensor input.



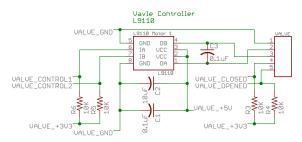

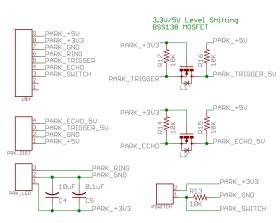
# Parking LED Ring

Distance sensor needs fast timing so can only be plugged into the top card slot and use Arduino pins directly instead of through shift registers. Pin 1/2 (Af/AF) are left open on the main connector to allow I2C pins to remain available for other sensors on the main board.



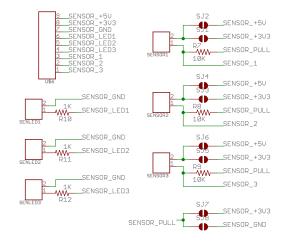
### Sensor Board

3 sensor inputs with pull up or down resistors. 3 LED outputs using 3V3 and 1k resistors. 3v/5v option on the sensor inputs because leak rope sensor requires 5v to function and works with 3v analog only inputs. NOTE: rope leak sensor requires analog input - work uth digital. During build, must solder jumper to select sensor power level and pull down/up.



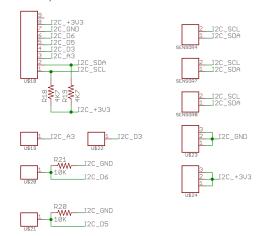
### I2C Board

3 I2C inputs with pull up resistors. Other pins are pass throughs. Only works on the top card slot, not through shift registers.



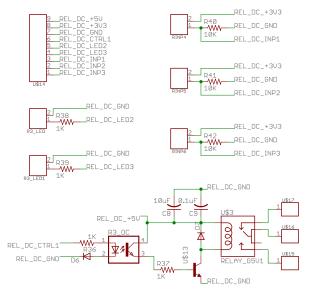
#### Relay DC

5V DC relay. 2 output LED's, 3 inputs will pull down resistors for suitches or sensors.


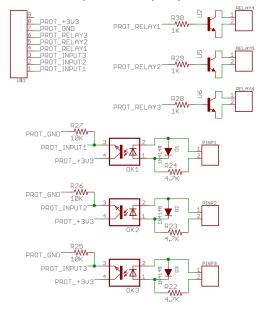
### Protected Input Board

3 transistor outputs for simple DC relay style suitching. 3 protected inputs for reading ~120 signal lines. Primary use for reading external PIR and camera signal wires and signalling cameras to record.



## Relay AC High Power

High power AC relay control with LED and switch with pull down resistor. Relay is 5V NO/NC.

